

# *A new DVCC-based fully cascadable voltage-mode full-wave rectifier*

Muhammed A. Ibrahim, · Erkan Yuce & · Shahram Minaei

Published in :

Journal of Computational Electronics (I.F.= 1.52)

Vol. 15, No. 3

First published online : 24 Aug 2016

# OUTLINE

- Abstract
- Introduction & Literature Survey
- Comparison of the proposed rectifier with the previously published ones
- Circuit description
- Simulation results
- Conclusion

# Abstract

- A new VM full-wave rectifier circuit employing two DVCC+ , two grounded resistors, and two diodes is proposed.
- The proposed circuit enjoys high input impedance and low output impedance; accordingly, it is suitable for direct cascading with other VM circuits
- It employs only two grounded resistors which are advantageous for IC implementations.
- However, it needs a single resistor matching condition.
- It is simulated using SPICE program to verify the theoretical analysis.

# Introduction & Literature Survey

- Rectifiers are widely used in a number of areas such as wattmeters, AC voltmeters and ammeters, RF demodulators, signal-polarity detectors, averaging circuits, peak-value detectors, piecewise linear function generators, and various nonlinear analog signal-processing circuits.
- The operation of diode-only rectifiers is limited by the threshold voltages of diodes, approximately 0.3 V for germanium diodes and 0.7 V for silicon diodes.

## **Introduction & Literature Survey (Cont'd)**

- Precision full-wave rectifiers using opamps were previously proposed.
- The action of the opamps effectively overcomes the threshold voltage of the rectifying diodes, which enables full-wave rectification of a low-level signal. However, the full-wave rectifiers based on opamps and diodes while generally are faster than other rectifier circuits suffer from a major disadvantage.

# Introduction & Literature Survey (Cont'd)

- The finite small-signal  $dV/dt$  of the opamps results in an important distortion of the rectified signal during the zero crossing of the input signal in which the nonconduction/conduction transition of the diodes occurs.
- Nevertheless, the use of the high slewrate opamps does not solve this drawback because of its zero transient problem.
- A number of circuits based on various active elements working in VM & CM for realizing full-wave rectification have been reported in the related literature.

# Comparison of the proposed rectifier with the previously published ones

VM full-wave rectifier	High input impedance	Low output impedance	Number of active elements	Number of resistors	Number of grounded resistors	Power diss (mW)
Ref. [2]	Yes	No	1 CCII+ current mirrors	2	2	NA
Ref. [3]	Yes	No	2 CCII	2	1	NA
Ref [4]	Yes	No	3 CCCII	5	2	NA
Ref. [5]	Yes	No	1 DO- OTA	1	1	NA
Ref. [6]	No	No	2 CCII 3 NMOS	0	0	NA
Ref. [7]	Yes	No	1 DXCCII 3 NMOS	0	0	3.33
Ref. [8]	Yes	Yes	1 CCII 1OA	3	2	NA
Ref. [9]	Yes	Yes	1 CCII 1 UVC	2	2	NA
Ref. [10]a	Yes	No	2 CCII	3	3	NA
Ref. [10]b	Yes	Yes	1 CCII 1 UVC	2	2	NA
Ref. [11]	Yes	No	2 CCII	3	1	NA
Ref. [12]	Yes	No	2 CCII	2	1	NA
Ref. [13]	No	Yes	2 DVCC 1 NMOS 1 VF	3	0	NA
Ref. [14]	No	No	1 CCII-	2	1	9.25
Ref. [15]	Yes	Yes	1 CCII 28 MOS	1	1	5.2
Proposed rectifier	Yes	Yes	2 DVCC+	2	2	0.93

# Circuit Description

$$\begin{bmatrix} I_{Y1} \\ I_{Y2} \\ V_X \\ I_{Z+} \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} V_{Y1} \\ V_{Y2} \\ I_X \\ V_{Z+} \end{bmatrix} \quad (1)$$

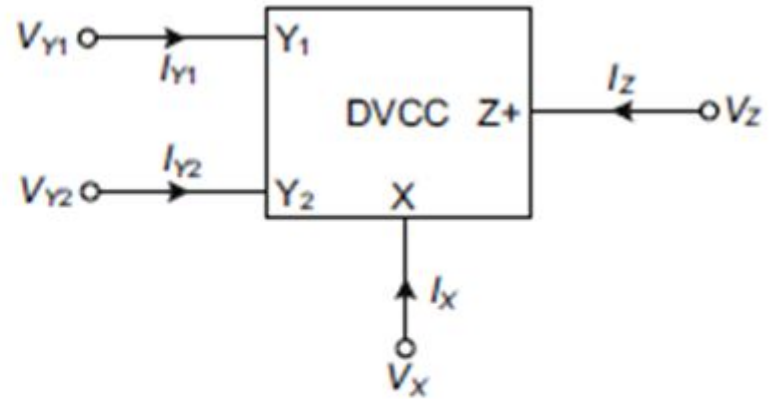


Fig. 1 Electrical symbol of the DVCC+

# Circuit description (Cont'd)

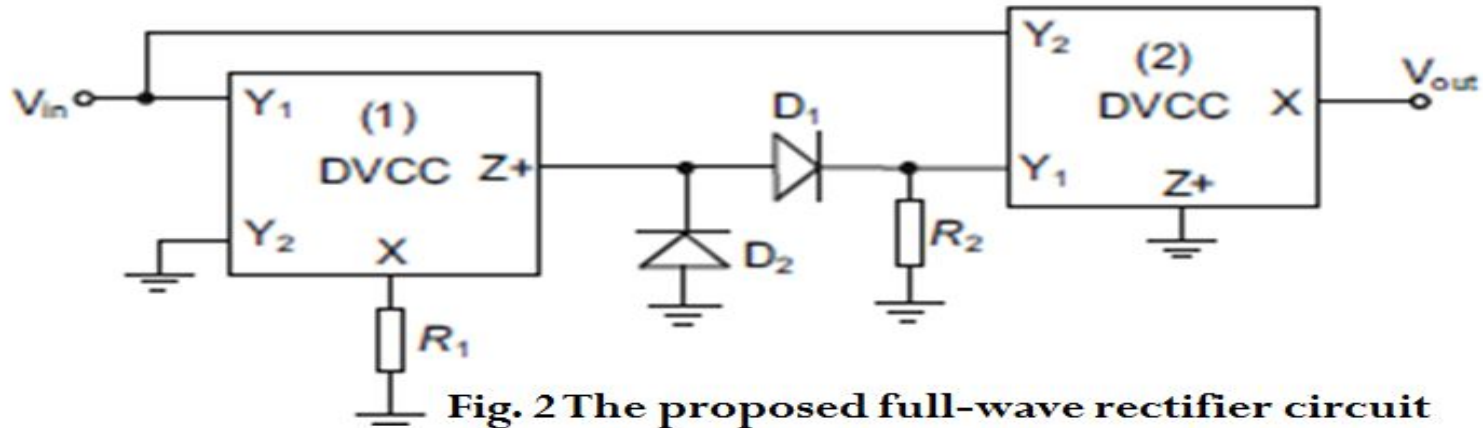


Fig. 2 The proposed full-wave rectifier circuit

$$V_{\text{out}} = \left( \frac{R_2}{R_1} - 1 \right) V_{\text{in}} \quad (2)$$

If  $R_2 = 2R_1$  is chosen in (2), we get

$$V_{\text{out}} = V_{\text{in}} \quad (3)$$

$$V_{\text{out}} = -V_{\text{in}} \quad (4)$$

Thus, for a full-wave input signal, we get

$$V_{\text{out}} = |V_{\text{in}}| \quad (5)$$

# Simulation Results

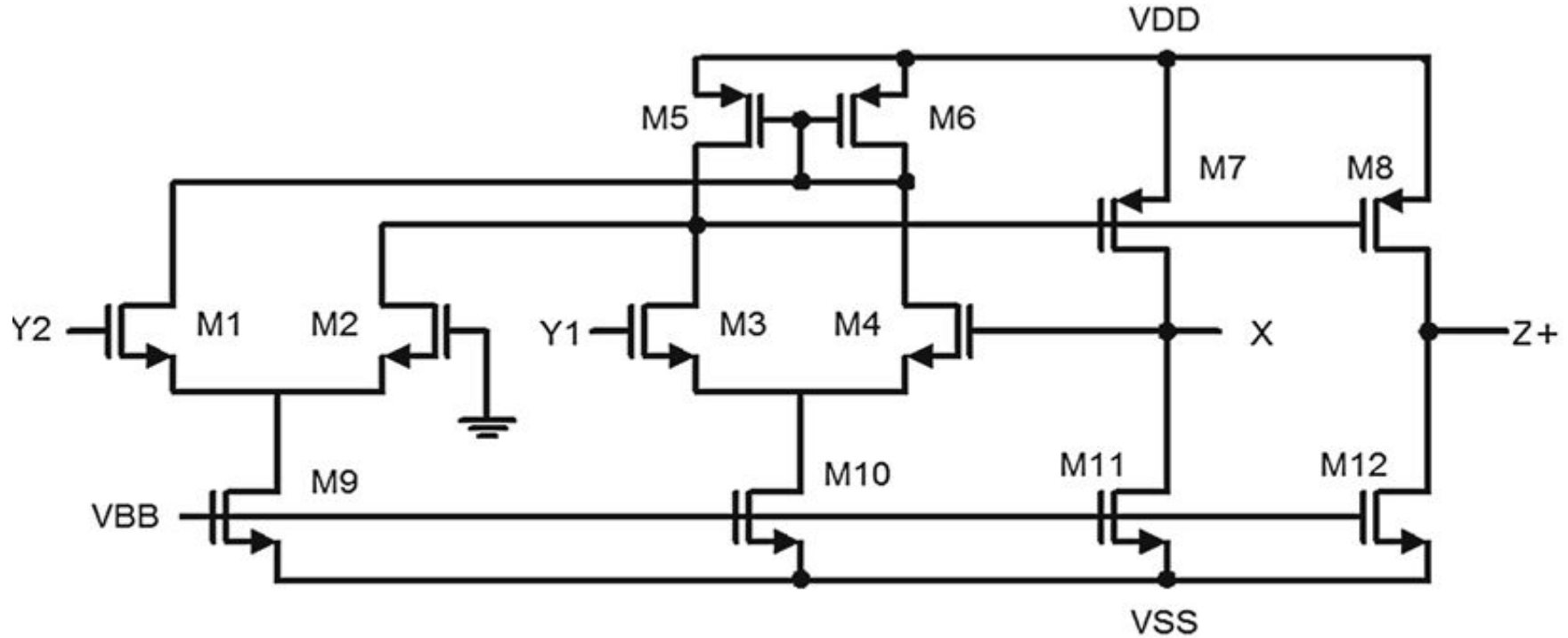


Fig. 4 The CMOS implementation of the DVCC+

# Simulation results (Cont'd)

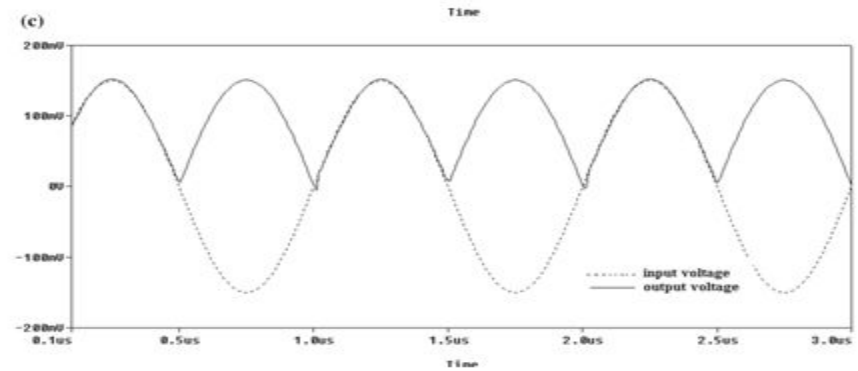
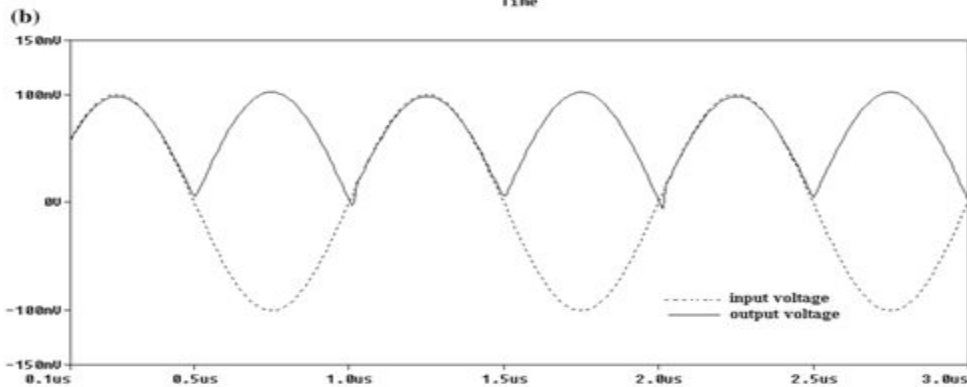
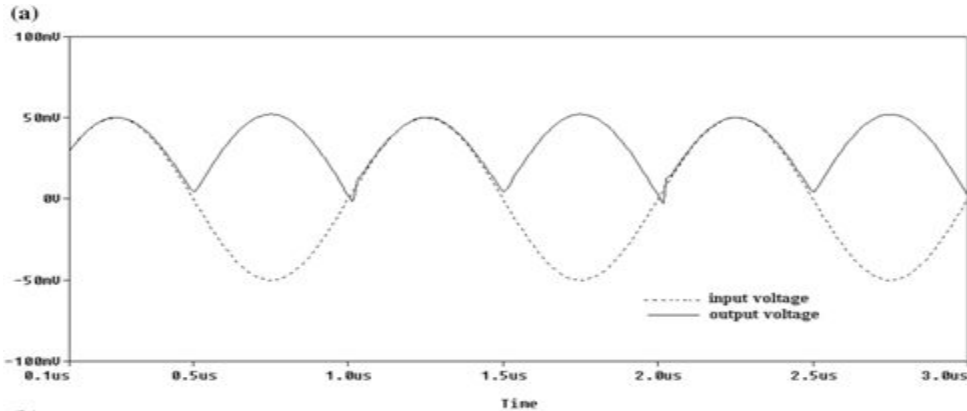


Fig. 10 Simulated transient response at  $f = 1$  MHz for  $V_p =$  a) 50 mV, b) 100 mV and c) 150 mV

# Simulation results (Cont'd)

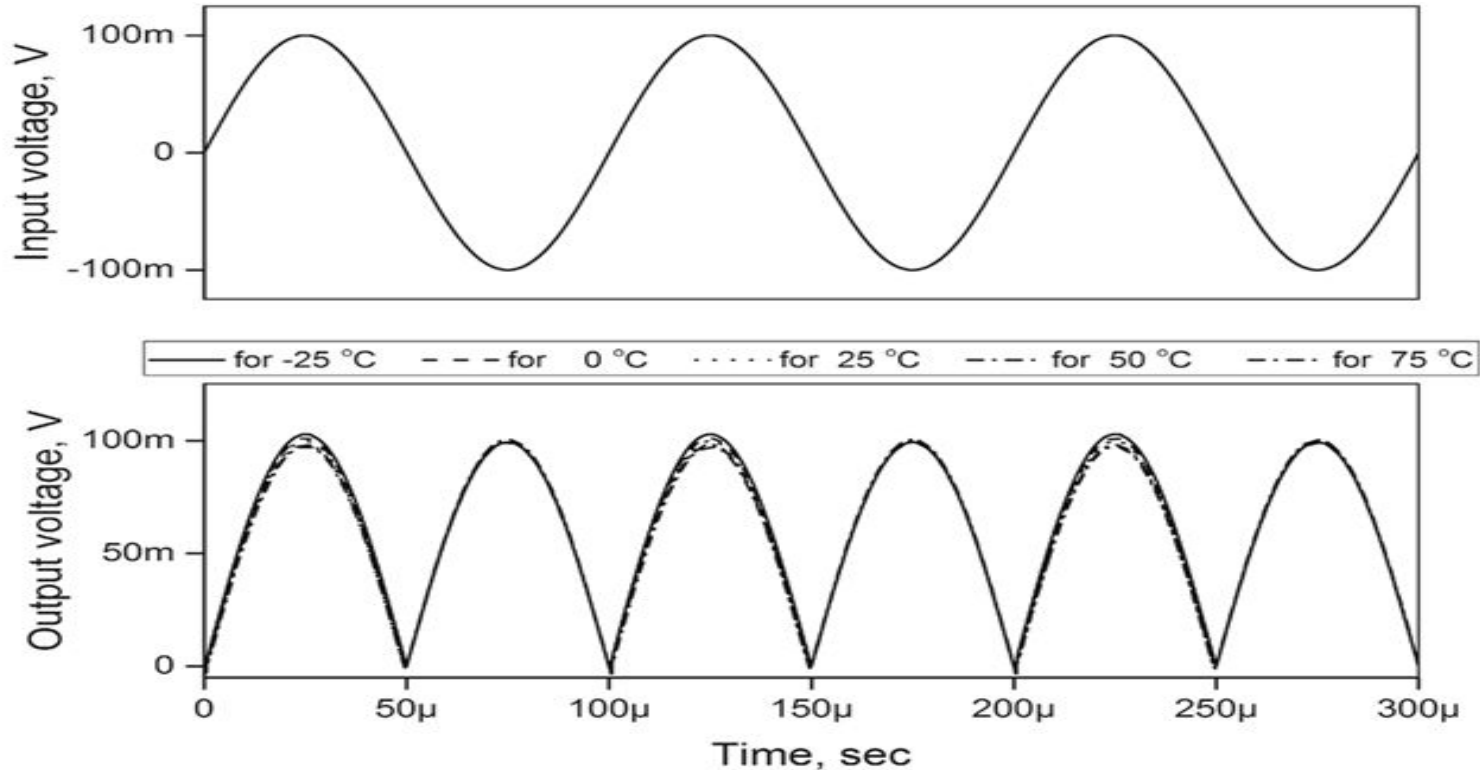


Fig. 13 Transient temperature analysis of the proposed full-wave rectifier circuit

# Simulation results (Cont'd)

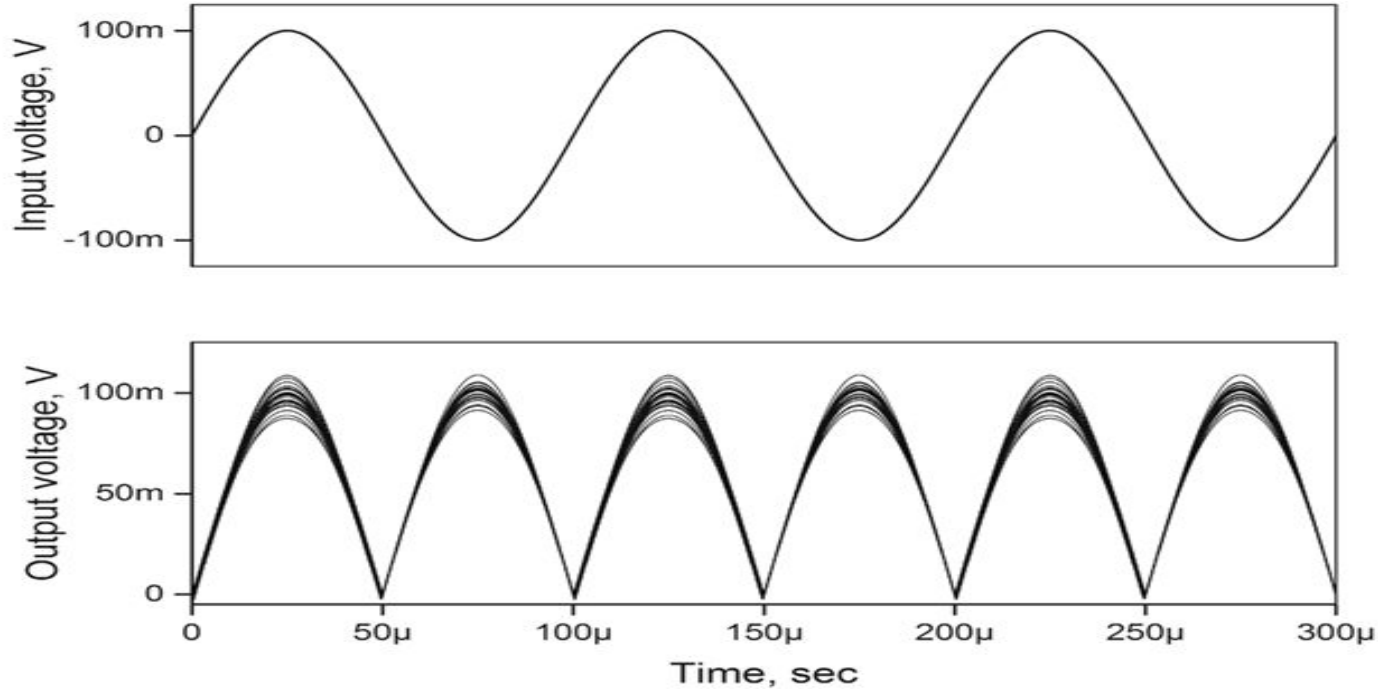


Fig. 14 Transient Monte Carlo analysis of the proposed full-wave rectifier structure

# Conclusion

- A new VM precision full-wave rectifier is proposed.
- It has the following features: high input impedance, low output impedance, the need to employ only two DVCC+s, two grounded resistors, and two diodes.
- To be easily cascaded with other VM circuits.
- The use of only grounded resistors is advantageous in IC circuit implementation and parasitic effect cancellation.
- The SPICE simulations confirm the effective operation of the proposed circuit in a wide frequency range.
- However, the difference between ideal and simulation results mainly stems from nonideal gains and parasitic impedances of the DVCC+s.
- It can be useful in many application fields such as signal processing, conditioning, and instrumentation of low-level signal, and DC converters.

Thank You

Questions?